

## Tutorial 4

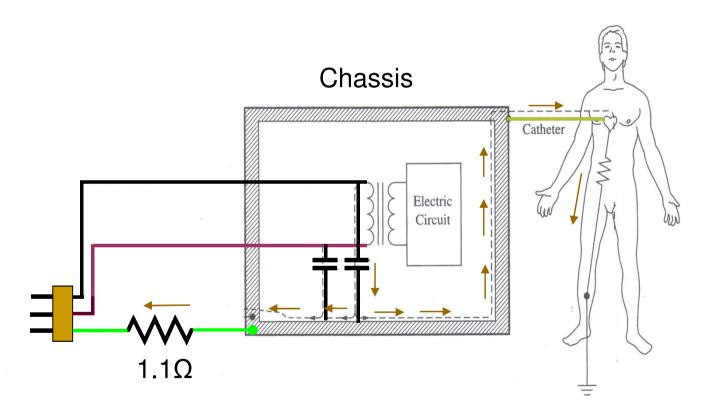**Question 1:** Suppose that the leakage current is 100  $\mu$ A. If the ground wire resistance is 1.1 $\Omega$  and a patient of 500- $\Omega$  resistance touches the instrument metal case, what is the body current?



## Solution:

The equivalent circuit of question 1 is

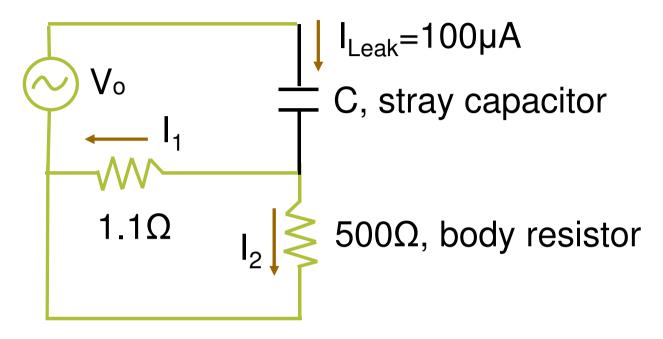


$$I_2 = \frac{1.1\Omega}{500\Omega + 1.1\Omega} \times 100\mu A = 0.2\mu A$$

$$I_2 = 0.2 \ \mu A, I_1 = 99.8 \ \mu A,$$

Question 2 A power engineer receives a lethal macroshock while standing in water and simultaneously touching the ungrounded metal casing on a high-voltage, 60-Hz power transformer. Assume that the resistance of the skin on the engineering's hand is 100 k $\Omega$  and the resistance of the skin on the engineer's feet is negligible. A capacitance of 25 nF is measurement between the transformer casing and the high-voltage conductors. Find the minimal value of the high voltage, assuming that 75 mA is the minimal fibrillating macroshock. Draw an equivalent circuit.

## **Solution:**

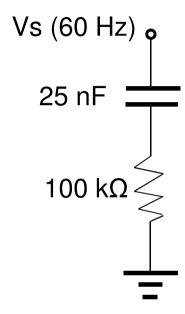


$$\frac{V_s}{75mA} \ge \left| R + \frac{1}{j\omega C} \right|$$
, and  $\omega = 2\pi \times 60 \ Hz$ 


$$\frac{V_s}{75mA} \ge \left(R^2 + \left(\frac{1}{\omega C}\right)^2\right)^{\frac{1}{2}} \ge (10^{10} + 1.1236 \times 10^{10})^{\frac{1}{2}} \ge 1.4573 \times 10^5$$

There for V<sub>s</sub>≥10929V

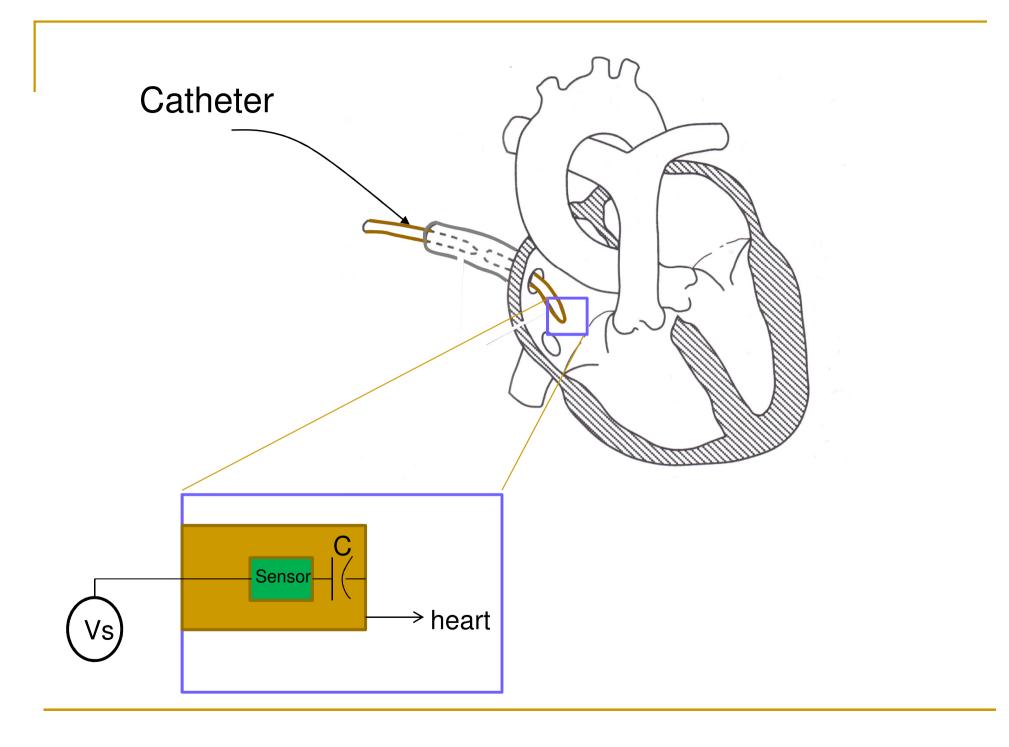Question 3 Calculate the maximal safe capacitance between a liquid-filled catheter and dc-isolated pressuresensor leads for a 120-V, 60-HZ fault in the sensor leads. Assuming that 10 uA is the minimal fibrillating microshock.



## **Solution:**

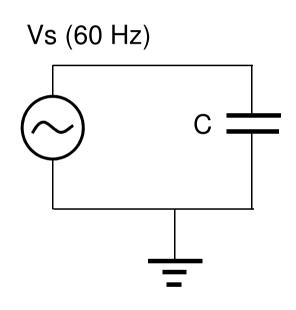

$$\begin{split} I_{VF} &= 10 \text{ uA}, \\ \frac{V_s}{I_{VF}} &< \left| R + \frac{1}{j\omega C} \right| \text{ , since body resistance} \\ &\text{is negligible} \end{split}$$

So 
$$\frac{V_s}{I_{VF}}$$
 = 120V/10uA<  $\left| \frac{1}{j\omega C} \right|$ ,

In which  $\omega = 2\pi \times 60 Hz$ ,

Therefore C < 220 pF